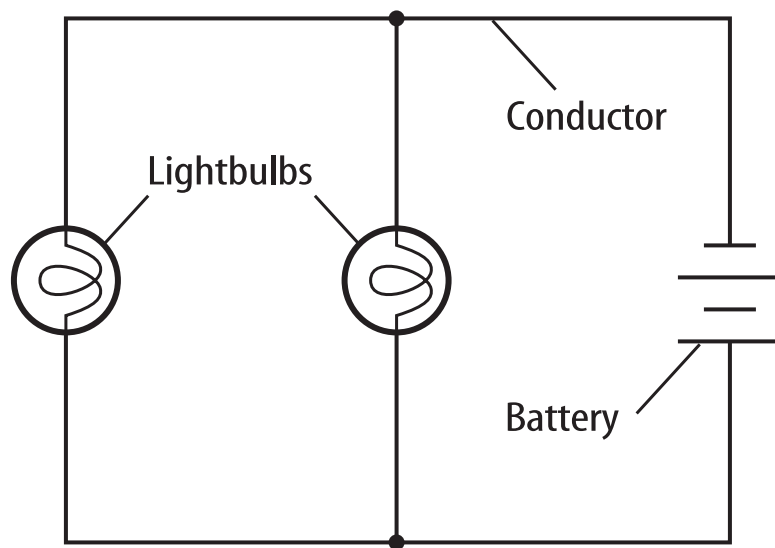
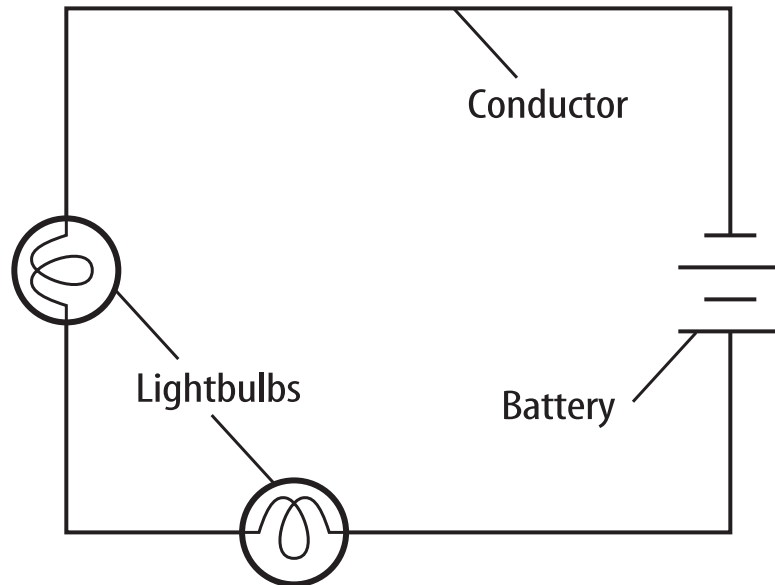


SECTION**1****Teaching Transparency
Activity****Series and Parallel
Circuits**

Teaching Transparency Activity (continued)

1. What is the main difference between a series circuit and a parallel circuit?

2. What kind of material makes up the object labeled “conductor” on the transparency?

3. Explain what happens in a series circuit if one of the lightbulbs stops shining.

4. If one lightbulb in a parallel circuit stops shining, how are the other lightbulbs connected in the circuit affected?

5. What kinds of circuits are used in the wiring of most homes?
