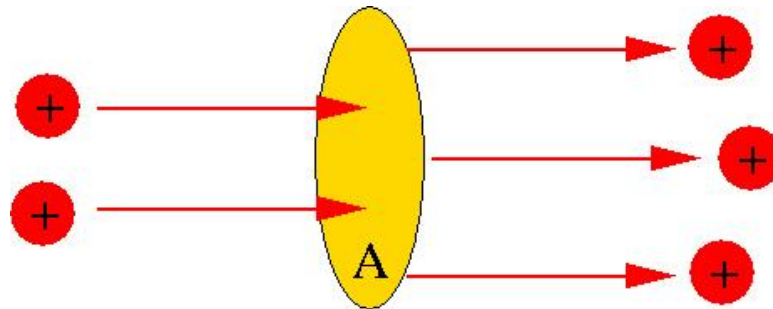


5 DC circuits

5.1 Electric current


- The current through a surface A is defined as the net charge that passes through the surface per second.

$$I = \frac{dQ}{dt} \quad (5.1)$$



where dQ is the amount of positive charge that passes through A .

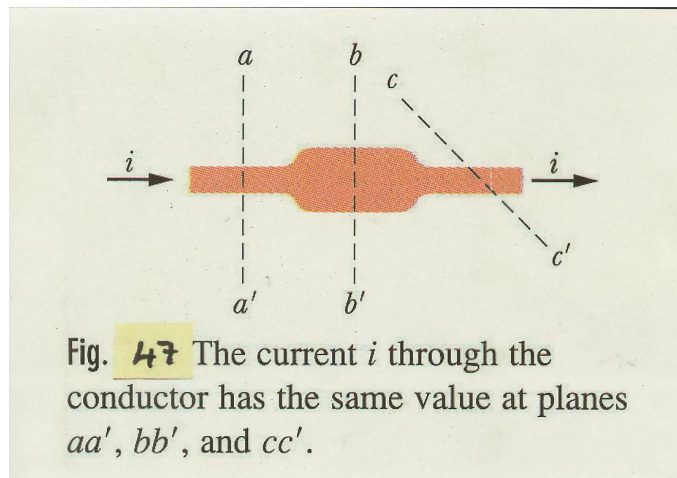
- Recall that in electrostatic equilibrium there are no electric fields or currents inside a conductor, so no moving charges. All charges are arranged on the surface. For currents to exist in the volume of a conductor, there must be a source of electric field that drives charges into motion and maintains that motion.



- Question: in the conductor shown in Figure 47, what current passes through the planes aa' , bb' , cc' ?
- Answer: the same current, because of charge conservation.

- The SI unit of current is the ampere (A): one ampere = one coulomb per second ($1 \text{ A} = 1 \text{ Cs}^{-1}$).

5.2 A microscopic model of current

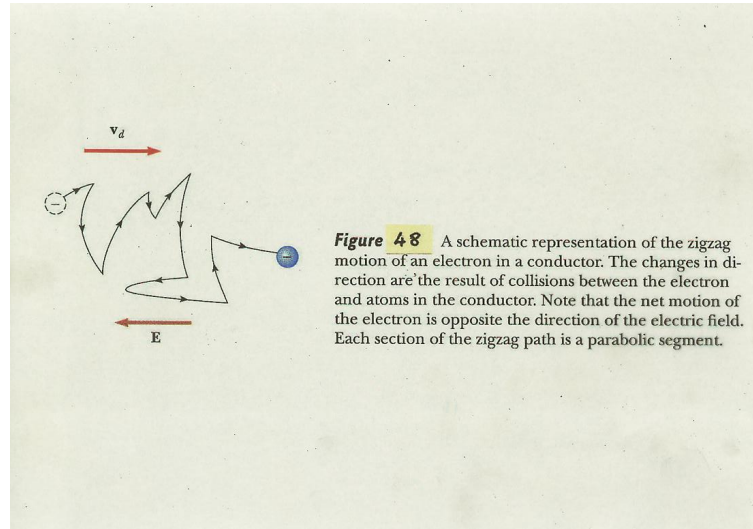

- Current flows if a potential difference (and hence an electric field $\underline{E}$) exists across a conductor. An electron responds by moving with a net drift velocity, $\underline{v}_d$ in the opposite direction to $\underline{E}$, as in Figure 48.
- Although it is electrons that move, conventionally we imagine equivalent positive charge carriers $+q$ moving with a velocity $\underline{v}_d$ parallel to $\underline{E}$.
- We define the **current density** as a vector in the direction of $\underline{v}_d$ whose magnitude is the net amount of charge crossing a unit area perpendicular to the drift velocity in unit time, so

$$\underline{J} = nq\underline{v}_d \quad (5.2)$$

with n the number of charge carriers per unit volume.

The current flowing through an area A is then

$$I = \int_A \underline{J} \cdot d\underline{a} \quad (5.3)$$

5.3 Ohm's law

Georg Ohm (1787-1854) found experimentally that for many materials, including most metals, the current density is proportional to the applied electric field,


$$\underline{J} = \sigma \underline{E} \quad (5.4)$$

where σ is a constant called the conductivity of the conductor. Equation 5.4 is called **Ohm's law**. The conductivity σ , as well as its inverse, the resistivity ρ , defined by

$$\rho = \frac{1}{\sigma} \quad (5.5)$$

does not depend on the geometry of the conductor but is a property of the material from which the conductor is made. Resistivity has units of ohm metres ($\Omega \text{ m}$). Some typical values are:

<u>Material</u>	<u>Resistivity, $\rho(\Omega \text{ m})$</u>
Copper	1.7×10^{-8}
Aluminium	2.82×10^{-8}
Iron	10×10^{-8}
Carbon	3.5×10^{-5}
(Glass)	10^{10} to 10^{14}

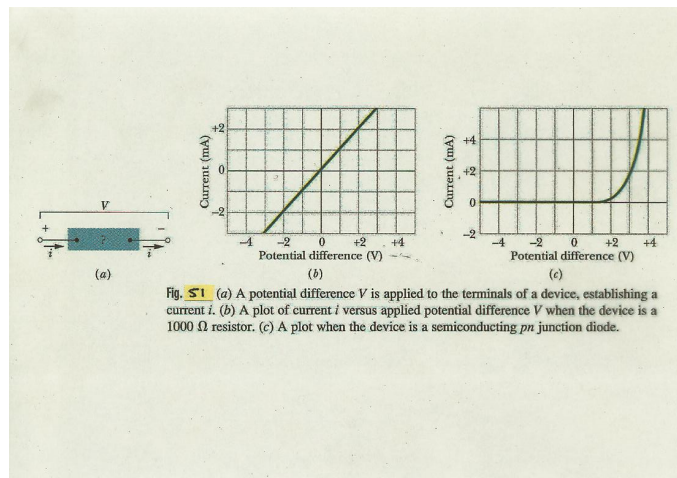


The final entry shows why glass is used as an electrical insulator on telephone poles etc.

- Ohmic materials are materials that obey Ohm's law - they include the resistors commonly used in electrical circuits.
- Non-ohmic materials include semiconductors (see Figure 51), frequently used in digital logic devices, such as pocket calculators.

Consider now the case of a wire of length l and cross-sectional area A . A uniform field $\underline{E}$ is associated with a constant potential difference ΔV :

$$E = \frac{\Delta V}{l} \quad (5.6)$$

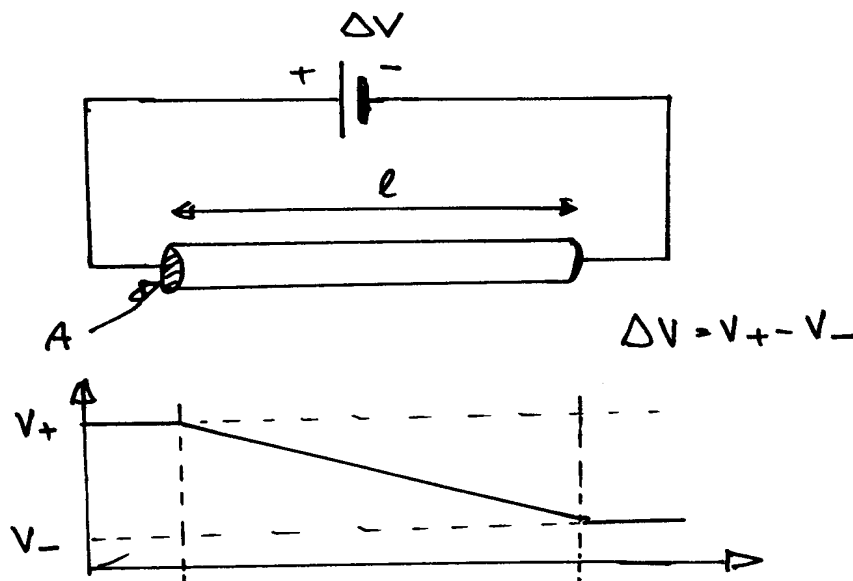(this comes from $\underline{E} = -\nabla V$ in one dimension, ie $E_x = -\frac{\partial V}{\partial x}$).



- Thus we have, combining 5.3, 5.4 and 5.6

$$J = \frac{I}{A} = \frac{\sigma \Delta V}{l} \quad (5.7)$$

$$\Delta V = I \left(\frac{l}{\sigma A} \right) = I R \quad (5.8)$$


where

$$R = \frac{l}{\sigma A} \quad (5.9)$$

is the resistance of the conductor. Its SI unit is the ohm (Ω). One ohm = one volt per ampere ($1\Omega = 1 \text{ V A}^{-1}$).

5.4 Electrical energy and power

- Consider the following circuit:

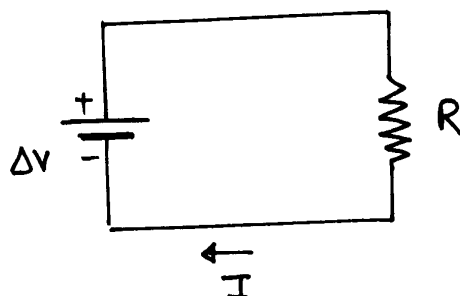

A battery connected by wires (of negligible resistance) to a resistor of resistance R , maintaining a potential difference ΔV across R . From Ohm's law a steady current I flows.

- The current I corresponds to the charge flowing per unit time, so in a time dt , a charge $dQ = Idt$ flows through the resistor R .
- This charge changes potential by ΔV as it moves through the resistor and therefore loses electric potential energy

$$dU = dQ\Delta V = Idt\Delta V \quad (5.10)$$

- We define power as the rate of change of potential energy,



$$P = \frac{dU}{dt} = I\Delta V \quad (5.11)$$

- In the circuit, chemical energy from the battery is continually being converted to internal thermal energy in the resistor. The course of an electron through R is like that of a stone falling through water at constant terminal speed. Its average kinetic energy is constant (current) but it loses potential energy to its surroundings. In the case of the electrons making up the current, the energy is lost by collisions with the (static) ions in the metal, generating heat.

- The unit of power is the watt (W): one watt = one volt-ampere = one joule per second ($1 \text{ W} = 1 \text{ V A} = 1 \text{ J s}^{-1}$).

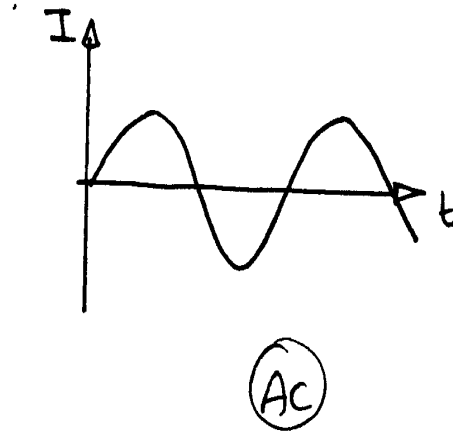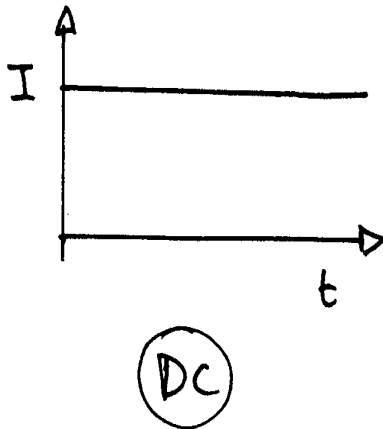5.5 AC and DC current

- ‘DC’ refers to ‘direct current’, as opposed to ‘alternating current’ (AC).




5.6 Pumping charges: EMF

- To maintain a constant current in a circuit we need a ‘charge pump’ to keep the potential difference between a pair of terminals. Examples of such pumps include batteries and electrical generators such as dynamos and solar cells.
- Consider a simple battery and resistor circuit:
- Charges (positive) flow clockwise, from the positive to negative battery terminals, through R . To pump charge (dq say) from the negative to positive terminals (ie inside the battery) requires work (dW say).
- We define the ‘EMF’ (symbol $\mathcal{E}$) of the battery to be the work done per charge:

$$\mathcal{E} = \frac{dW}{dq} \quad (5.12)$$

where EMF stands for ‘electromotive force’ the ‘force’ that makes the charges move.

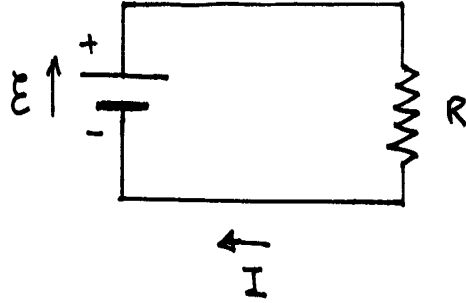- Equation 5.12 is essentially the same as the definition of potential difference ΔV . Note that $\mathcal{E}$ is therefore not a force but a potential difference.



5.7 Single-loop circuits

- We can apply the principle of conservation of energy to allow us to calculate currents in a circuit.
- In section 5.4 we saw that power

$$P = \frac{dW}{dt} = I \Delta V \quad (5.13)$$

- In the circuit above $\Delta V = I R$, so

$$P = I^2 R \quad (5.14)$$

is the rate of energy dissipation in the resistor. Substituting in equation 5.13 we have for the energy dissipated in a time dt ,

$$dW = I^2 R dt \quad (5.15)$$

$$= \mathcal{E} dq \quad (5.16)$$

$$= \mathcal{E} I dt \quad (5.17)$$

$$\therefore \mathcal{E} I = I^2 R \quad (5.18)$$

$\mathcal{E} = I R \quad (5.19)$

- The (chemical) energy per charge gained in the battery equals the (thermal) energy per charge dissipated in the resistor.

- Another way of expressing this is to say that “the sum of all potential differences around any closed circuit loop must be zero”

$$\sum_{\text{closed loop}} \Delta V = 0 \quad (5.20)$$

which is known as Kirchhoff’s loop rule.


- In the simple circuit composed of a resistor and a battery, this is simply

$$\mathcal{E} - IR = 0 \quad (5.21)$$

$$\therefore \mathcal{E} = IR \quad (5.22)$$

as in equation 5.19

- For resistors in series

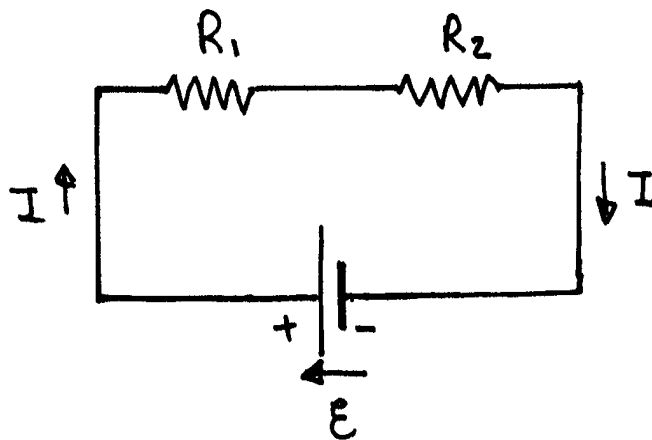


Kirchhoff’s loop rule gives

$$\mathcal{E} - IR_1 - IR_2 = 0 \quad (5.23)$$

which is like equation 5.19 with $R_{\text{equivalent}} = R_1 + R_2$. In general for resistors wired in series

$$R_{\text{equivalent}} = \sum_i R_i \quad (5.24)$$

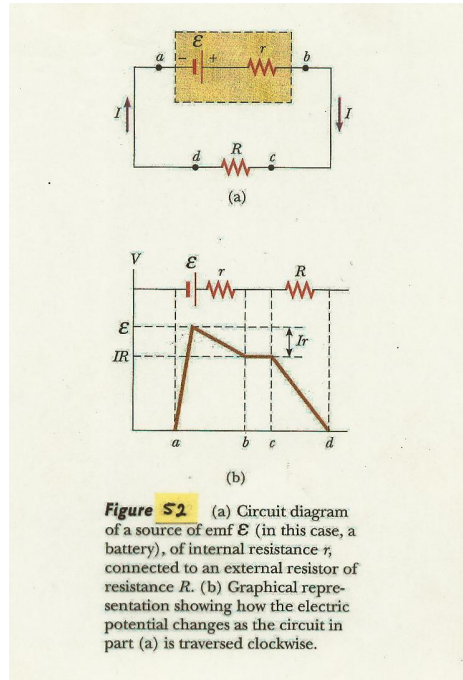- The change in electric potential around such a circuit is illustrated in Figure 52.




5.8 Multi-loop circuits

- What is the equivalent resistance for a circuit with resistors in parallel?
- We note first that the potential differences across R_1 and R_2 are the same.
- We next note that “The sum of the currents entering any junction in a circuit must equal the sum of currents leaving it”

$$\sum I_{\text{in}} = \sum I_{\text{out}} \quad (5.25)$$

which is Kirchhoff’s junction rule. It follows from the conservation of charge in the circuit.

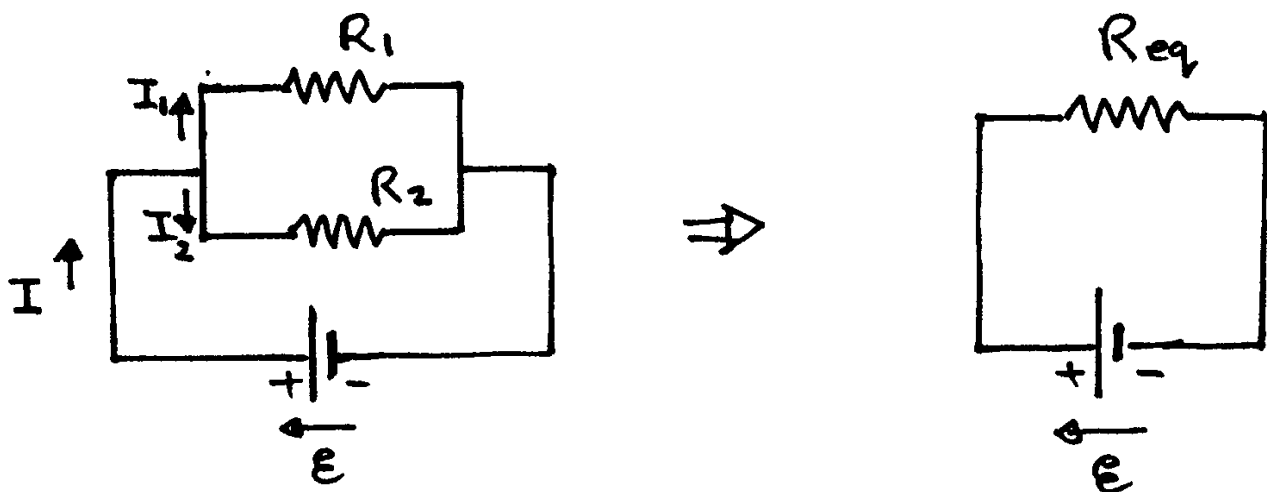- So in the circuit considered above, and consisting of two resistors in series and a



battery, we have:

$$I = I_1 + I_2 \quad (5.26)$$

$$= \frac{\Delta V}{R_1} + \frac{\Delta V}{R_2} \quad (5.27)$$

$$= \Delta V \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \quad (5.28)$$

$$= \Delta V \frac{1}{R_{\text{eq}}} \quad (5.29)$$

$$\therefore \frac{1}{R_{\text{eq}}} = \frac{1}{R_1} + \frac{1}{R_2} \quad (5.30)$$


or, in general,

$$\frac{1}{R_{\text{equivalent}}} = \sum_i \frac{1}{R_i} \quad (5.31)$$

for a collection of resistors wired in parallel.

5.9 Time-varying currents

Figure 53 shows an ‘RC series circuit’, a resistor and a capacitor in series.

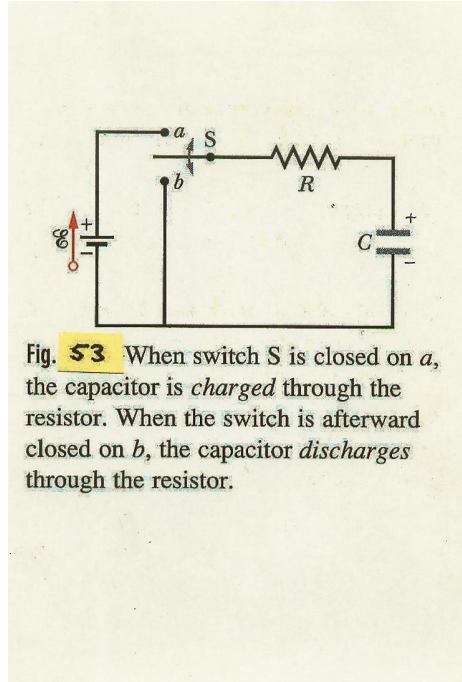

- To charge the capacitor C from zero, we close the switch S to point a . From Kirchhoff's loop rule

$$\mathcal{E} - IR - \frac{q}{C} = 0 \quad (5.32)$$

where $I = I(t)$ and $q = q(t)$ both vary with time and across the capacitor $\Delta V = \frac{q}{C}$. Note that the potential decreases on going from the positive to the negative plate of the capacitor. We also have $I = \frac{dq}{dt}$, so equation 5.32 becomes

$$\frac{dq}{dt} + \left(\frac{1}{RC} \right) q = \frac{\mathcal{E}}{R} \quad (5.33)$$


which has the solution

$$q(t) = C\mathcal{E} \left(1 - e^{-\frac{t}{RC}} \right) \quad (5.34)$$

from which we can derive the current

$$I(t) = \frac{dq}{dt} = \frac{\mathcal{E}}{R} e^{-\frac{t}{RC}} \quad (5.35)$$

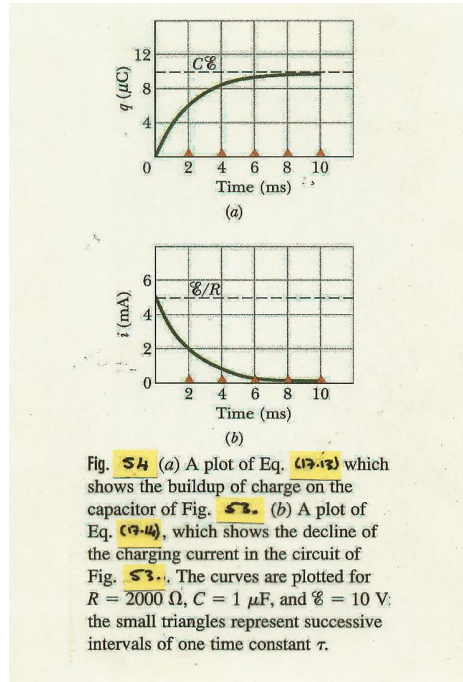where RC is the time constant of the circuit.



- Plots of $q(t)$ and $I(t)$ are shown in Figure 54.
- Note that at the time $t = RC$,

$$\frac{I(t = RC)}{I(t = 0)} = \frac{\frac{\mathcal{E}}{R}e^{-1}}{\frac{\mathcal{E}}{R}} = \frac{1}{e} = 0.368 \quad (5.36)$$

- The units of RC are $\Omega \text{ F} = \text{V A}^{-1} \text{ C V}^{-1} = \text{V C}^{-1} \text{ s C V}^{-1} = \text{s}$