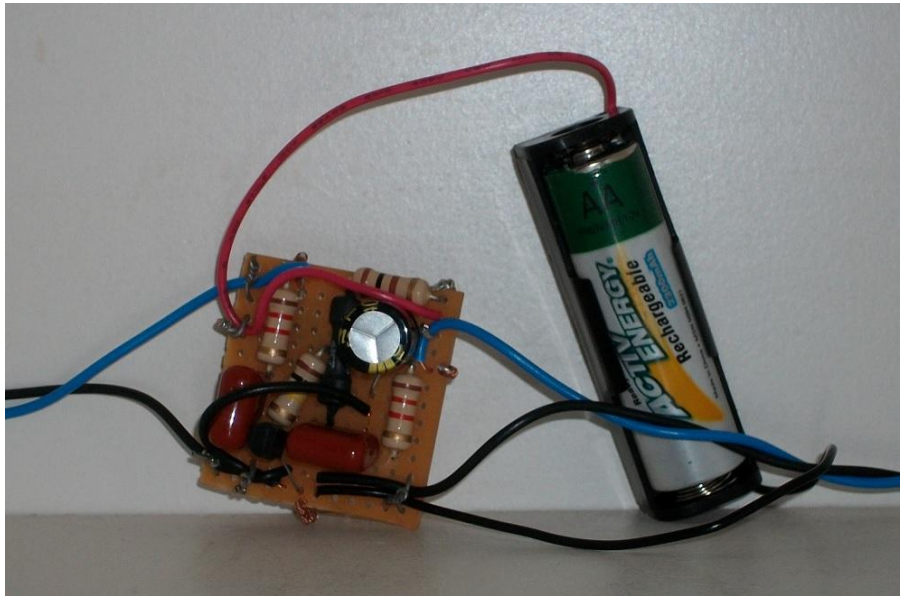


# Transistor Amplifier

## 1. Introduction

This article is about a simple feedback bias transistor amplifier circuit.




**Figure 1:** Feedback Bias Transistor Amplifier

Nowadays you can purchase instrumentation amplifiers for a very low cost. Well known companies include Maxim Integrated, Texas Instruments and Analog Devices.

Of all the one transistor amplifier configurations, this one is the most complicated.

## 2. Step 1: Design the Circuit

The design of the circuit is very simple:

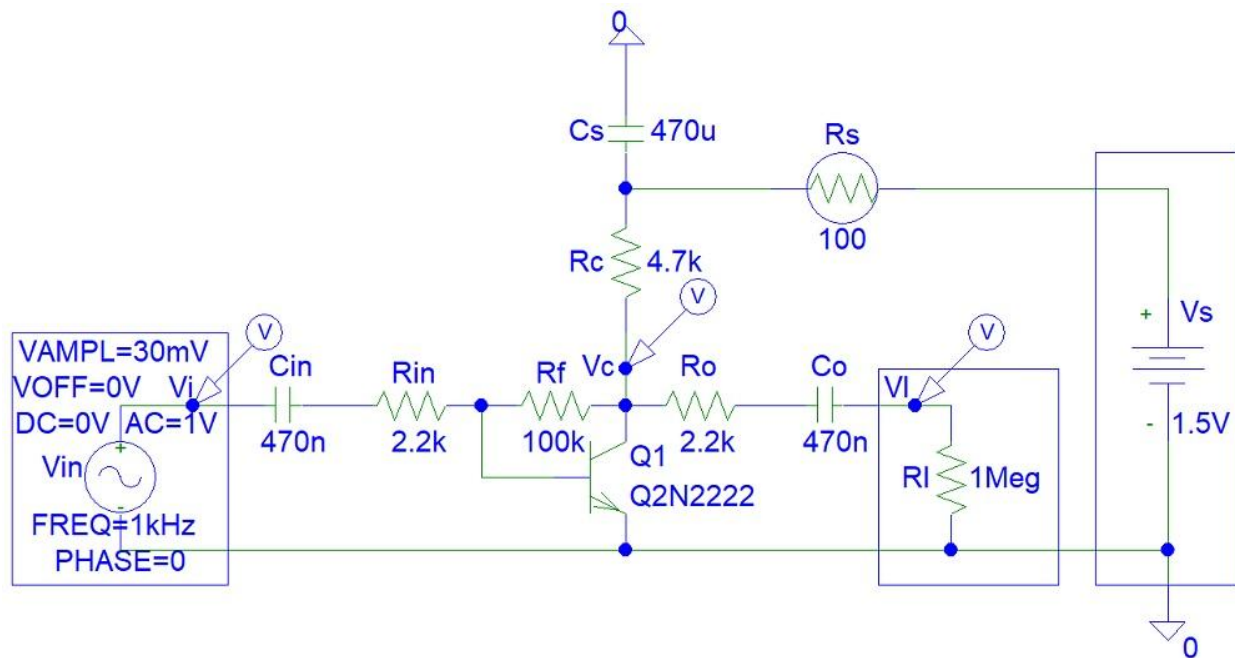

**Figure 2:** Feedback Bias Transistor Amplifier Design

Calculate the collector biasing voltage:

$$V_c = V_s - I_c \cdot R_c$$

$$= V_s - \beta \cdot I_b \cdot R_c$$

$$= V_s - \beta \cdot \left( \frac{V_c - V_{be}}{R_b} \right) \cdot R_c$$

$$V_s = V_c + \beta \cdot \left( \frac{V_c - V_{be}}{R_b} \right) \cdot R_c$$

$$V_s \cdot R_b / R_c / \beta = V_c \cdot R_b / R_c / \beta + V_c - V_{be}$$

$$V_s \cdot R_b / R_c / \beta + V_{be} = V_c \cdot R_b / R_c / \beta + V_c$$

$$V_s \cdot R_b / R_c / \beta + V_{be} = V_c \cdot (R_b / R_c / \beta + 1)$$

$$V_c = (V_s \cdot R_b / R_c / \beta + V_{be}) / (R_b / R_c / \beta + 1)$$

$$= (V_s + V_{be} \cdot \beta \cdot R_c / R_b) / (1 + \beta \cdot R_c / R_b)$$

$V_{be}$  is usually about 0.7 V. If  $V_{be}$  is small in value when compared to  $V_s$  then:

$$V_c = V_s / (1 + \beta \cdot R_c / R_b)$$

$$1 + \beta \cdot R_c / R_b = V_s / V_c$$


$$R_c / R_b = (V_s / V_c - 1) / \beta$$

$$R_b / R_c = \beta / (V_s / V_c - 1)$$


You can Google feedback bias transistor amplifier design for more information.

### 3. Step 2: Simulations

Simulations show a how the transistor is amplifying the signal with a 1 Megohm load:

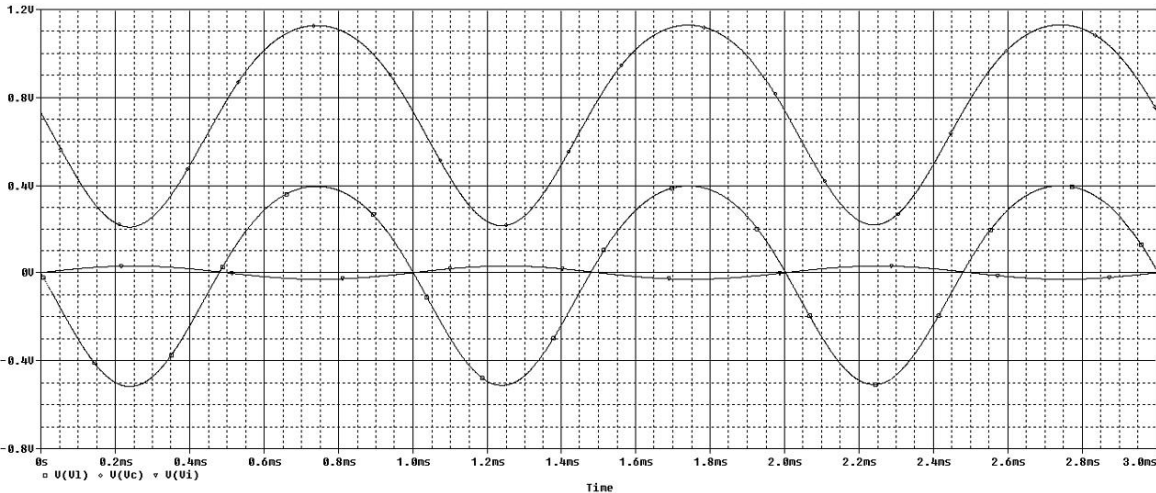

**Figure 3:** Feedback Bias Transistor Amplifier Transient Simulations

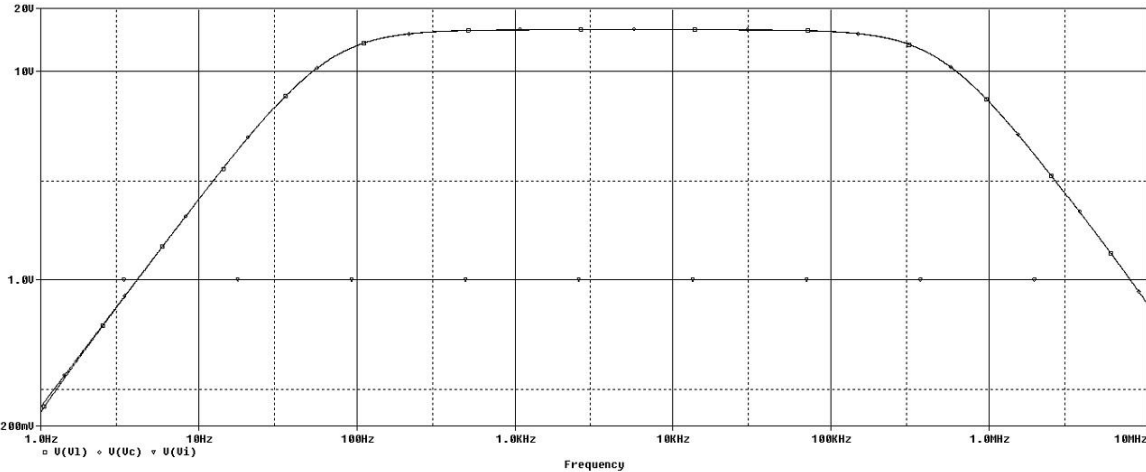


**Figure 4:** Feedback Bias Transistor Amplifier Frequency Simulations

A general purpose transistor would not have such wide bandwidth in practice.

## 4. Step 3: Make the Circuit

I made the circuit on a very small matrix board:

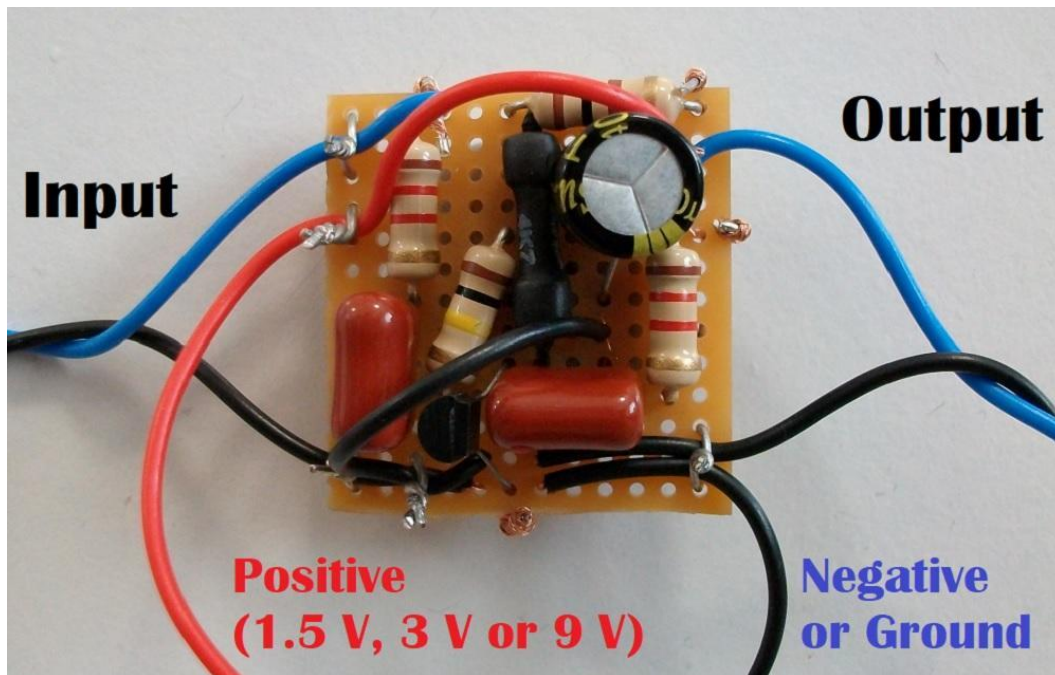

**Figure 5:** Building the Circuit

I should have used a bigger matrix board. However, this is what I had in stock.

## 5. Step 4: Testing

I used an Instrustar USB oscilloscope for testing. The red curve is the input and the green is the output.

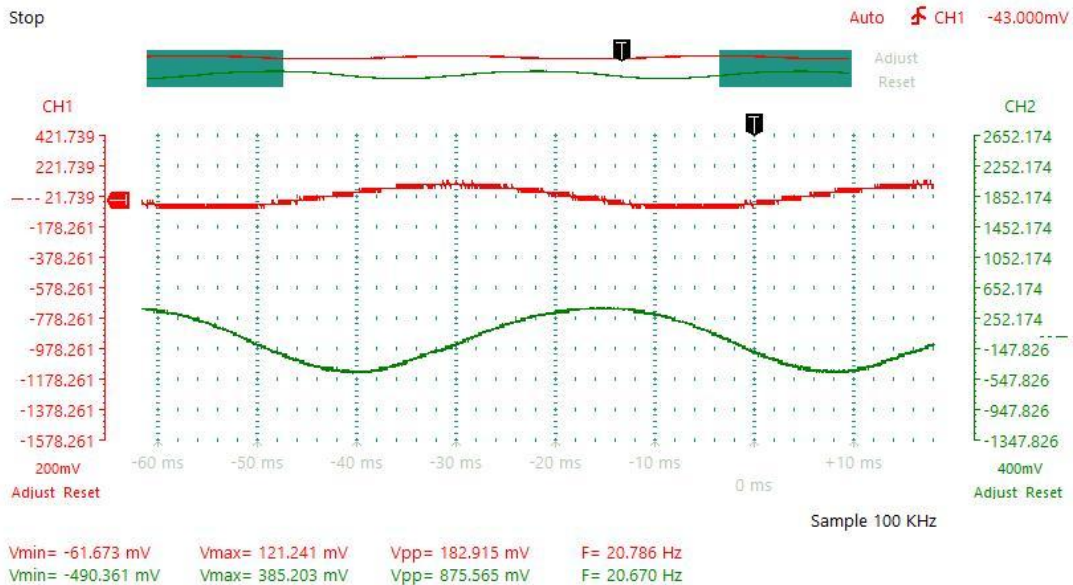


Figure 6: 20 Hz Input

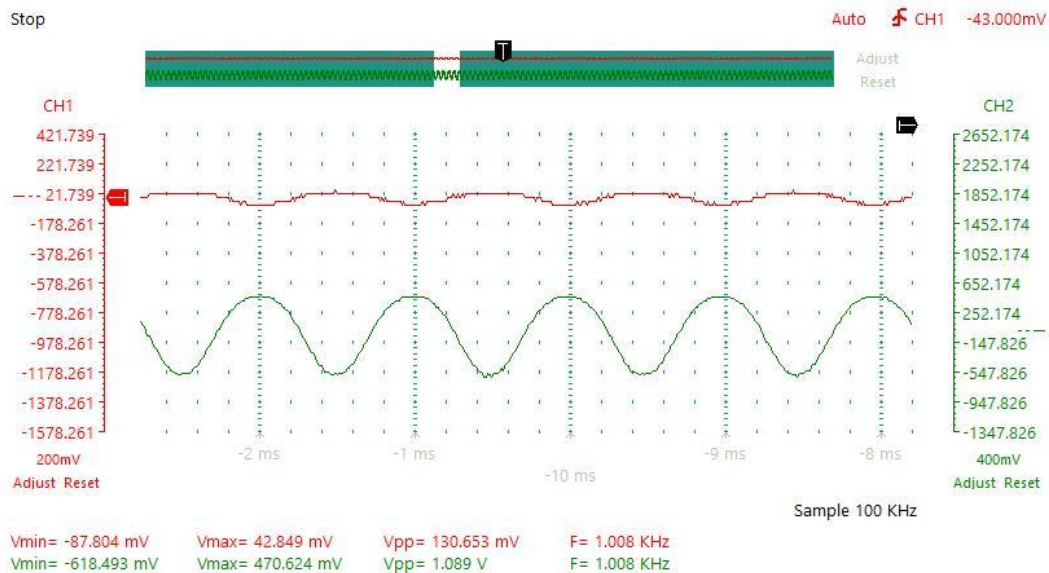


Figure 7: 1 kHz Input

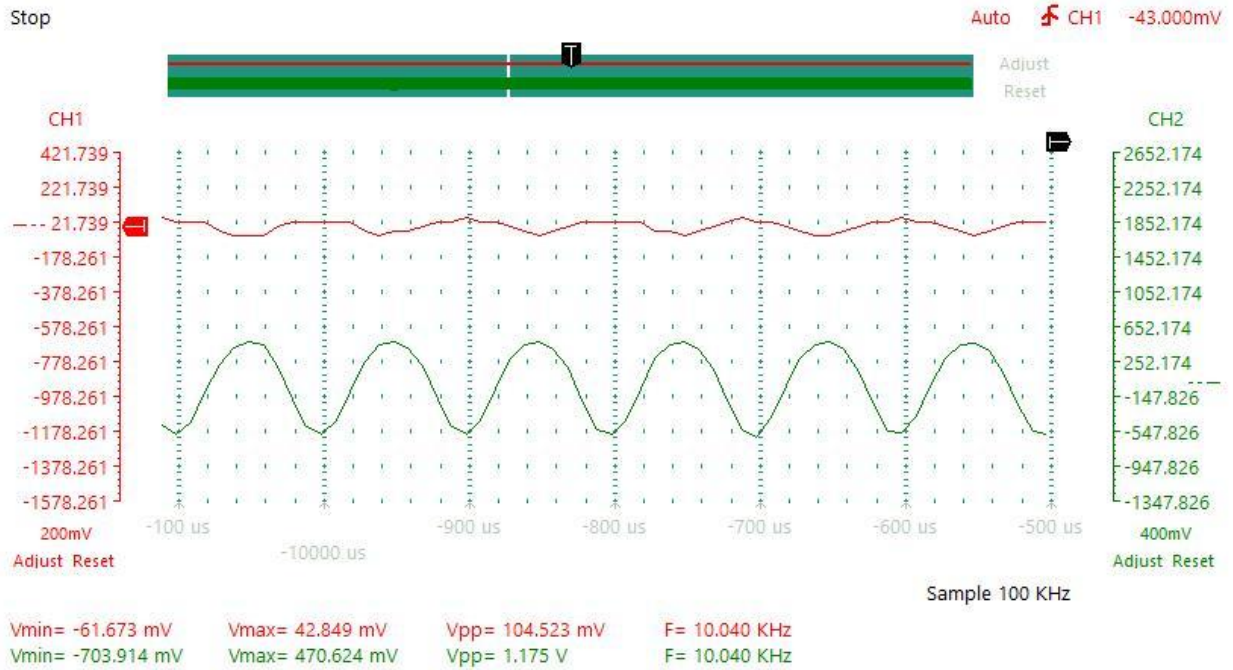


Figure 8: 10 kHz Input


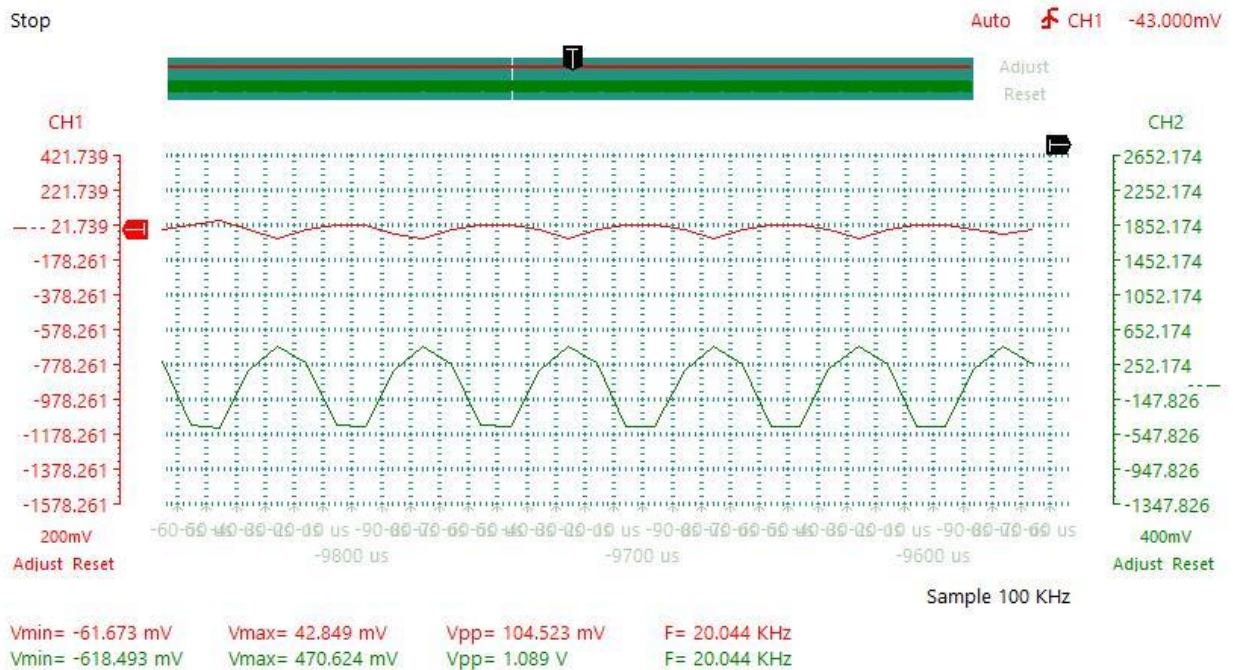


Figure 9: 20 kHz Input

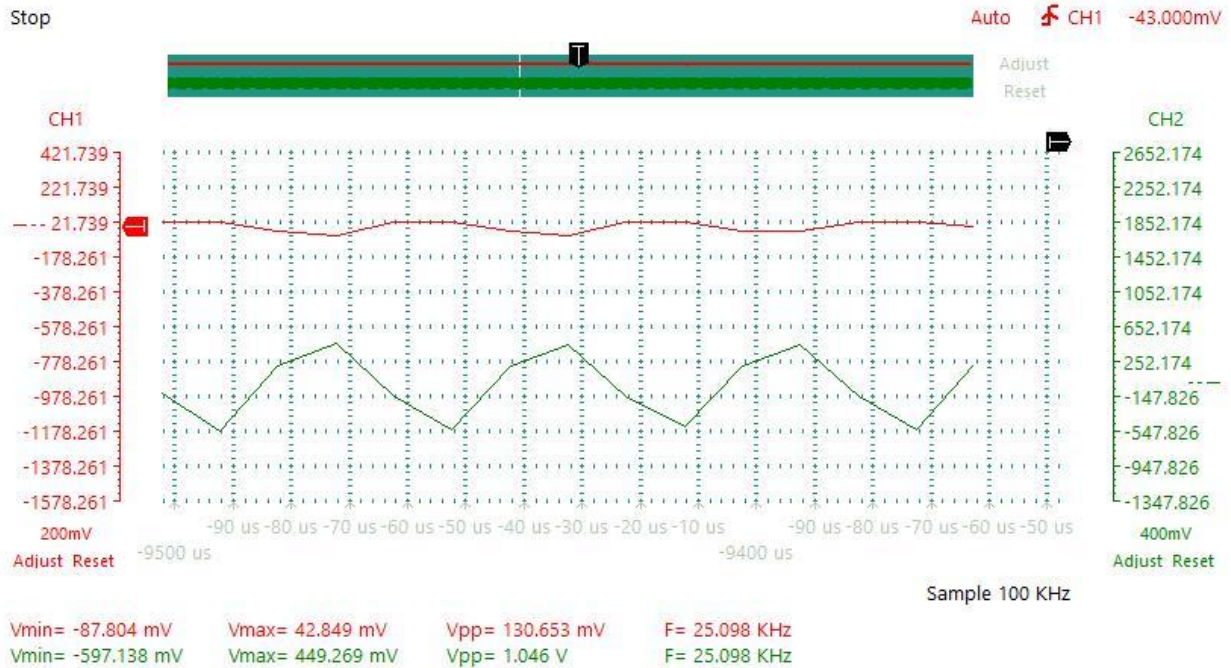

**Figure 10: 25 kHz Input**

Testing showed that the feedback transistor amplifier has a lower gain than a fixed bias transistor amplifier:

## 6. Conclusion

Other transistor amplifiers include fixed bias and stabilised bias configurations that you can research on the internet.



## 7. References

1. <https://www.allaboutcircuits.com/textbook/semiconductors/chpt-4/biasing-calculations/>
2. [https://en.wikipedia.org/wiki/Bipolar\\_transistor\\_biasing](https://en.wikipedia.org/wiki/Bipolar_transistor_biasing)